

# The Right Timing

Frederik Dostal  
Analog Devices, Inc.

Many analog circuits need a type of clock signal or a possibility of executing a task after a certain time. There are various solutions available for such applications. For simple timing tasks, a standard 555 circuit can be used. With the 555 circuit and the appropriate external components, numerous different tasks can be performed.

One disadvantage of the popular 555 timer, however, is the inaccuracy of the timer setting. A 555 timer works through charging an external capacitor and detecting a voltage threshold. This circuit is very easy to create, but its accuracy depends strongly on the actual value of its capacitor.

Crystal oscillators lend themselves well to applications requiring higher accuracies. Their accuracy may be high, but they show weakness in another area: reliability. Anybody involved in repairing electrical equipment knows that failure is usually caused by large, predominantly electrolytic capacitors. Crystal oscillators represent the second most frequent cause of failure.

The third way of measuring lengths of time or generating clock signals is with a simple, small microcontroller. Here, too, there is a large selection of components with different optimizations available. However, they need to be programmed, their handling requires a somewhat more in-depth understanding, and they must be scrutinized carefully in critical applications due to their digital design—for example, what occurs in the system if the microcontroller gets stuck.

Apart from these three basic building blocks for clock generation, there are other, less well-known alternatives. The TimerBlox modules from Analog Devices constitute one such alternative. They are silicon-based timing modules that, unlike microcontrollers, are fully analog in operation and can be adjusted via resistors. Thus, software programming is not necessary and the function is very reliable. Figure 1 shows an overview of the different TimerBlox modules with their respective basic functions. Countless other functions can be generated with these basic building blocks.

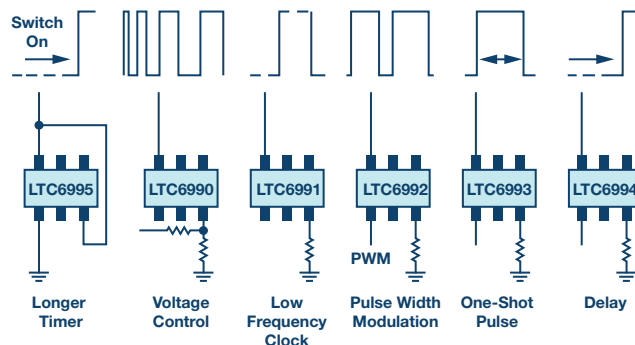


Figure 1. TimerBlox circuits for generating different timing functions.

In contrast to the widely used 555 timer circuits, the TimerBlox circuits do not depend on the charging of an external capacitor. All settings are made with resistors and the function is therefore more precise. Accuracies of 1% to 2% can be realized. Crystal oscillators have an even higher accuracy of about a factor of 100, but this comes with the disadvantages such a solution brings.

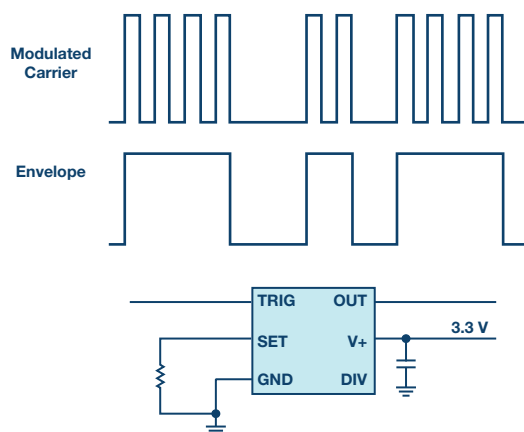


Figure 2. Envelope detector with an LTC6993 TimerBlox integrated circuit.

The applications for timing blocks are very diverse. Numerous example circuits have been published by Analog Devices. Figure 2 shows an envelope detector. Several fast pulses are combined to form a longer pulse. The external components of the LTC6993-2 are minimal for this application. The capacitor in the circuit is just a backup capacitor for supporting the supply voltage and has no effect on the accuracy of the timing module.

Other interesting applications include phase-shifted synchronization of multiple switching regulators for power supplies or the addition of spread spectrum modulation to a switching regulator IC with synchronization input. Another typical application is the provision of a defined delay, that is, the function of a timer for switch-on delays for specific circuit segments.

There are numerous different technical solutions for generating a clock signal and performing various time-based tasks. Each of them has advantages and disadvantages. Silicon oscillators such as the TimerBlox modules are characterized by ease of operation, high accuracy due to the use of variable resistors instead of capacitors, and excellent reliability.

### About the Author

Frederik Dostal studied microelectronics at the University of Erlangen-Nuremberg, Germany. Starting work in the power management business in 2001, he has been active in various applications positions, including four years in Phoenix, Arizona, working on switch mode power supplies. He joined Analog Devices in 2009 and works as a power management technical expert for Europe. He can be reached at [frederik.dostal@analog.com](mailto:frederik.dostal@analog.com).

### Online Support Community



Engage with the Analog Devices technology experts in our online support community. Ask your tough design questions, browse FAQs, or join a conversation.

Visit [ez.analog.com](http://ez.analog.com)

#### Analog Devices, Inc. Worldwide Headquarters

Analog Devices, Inc.  
One Technology Way  
P.O. Box 9106  
Norwood, MA 02062-9106  
U.S.A.  
Tel: 781.329.4700  
(800.262.5643, U.S.A. only)  
Fax: 781.461.3113

#### Analog Devices, Inc. Europe Headquarters

Analog Devices GmbH  
Ott-Aicher-Str. 60-64  
80807 München  
Germany  
Tel: 49.89.76903.0  
Fax: 49.89.76903.157

#### Analog Devices, Inc. Japan Headquarters

Analog Devices, KK  
New Pier Takeshiba  
South Tower Building  
1-16-1 Kaigan, Minato-ku,  
Tokyo, 105-6891  
Japan  
Tel: 813.5402.8200  
Fax: 813.5402.1064

#### Analog Devices, Inc. Asia Pacific Headquarters

Analog Devices  
5F, Sandhill Plaza  
2290 Zuchongzhi Road  
Zhangjiang Hi-Tech Park  
Pudong New District  
Shanghai, China 201203  
Tel: 86.21.2320.8000  
Fax: 86.21.2320.8222

©2019 Analog Devices, Inc. All rights reserved. Trademarks and registered trademarks are the property of their respective owners. Ahead of What's Possible is a trademark of Analog Devices. TA21281-5/19

[analog.com](http://analog.com)



AHEAD OF WHAT'S POSSIBLE™