

## APPLICATION NOTE 4983

## Wide Input Flyback Converter Features 5V at 2.6A Output

*Abstract: This reference design is for a highly efficient, flyback, 5V Class 3 powered device (PD) with a wide 9V to 57V auxiliary input. The design features the MAX5969B as its controller. The design also uses the MAX5974D, which controls current-mode PWM converters and provides frequency foldback for both the auxiliary input and power over Ethernet (PoE) applications. Using these devices, this reference design is IEEE® 802.3af/at compliant. It is also a high-performance, compact, and cost efficient solution for a Class 3 PD. The design can also support the wide auxiliary-input voltage range to provide 10W output power.*


## General Description

This reference design features the [MAX5969B](#) and [MAX5974D](#). The MAX5969B controller is fully compliant with the IEEE 802.3af/at standard in a power-over-Ethernet (PoE) system. The device can also be powered from a wall adapter (WAD). The MAX5974D controls wide 9V to 57V input-voltage, active-clamped, current-mode PWM converters and provides frequency foldback. Using these devices, this reference design is IEEE 802.3af/at compliant. It is also a high-performance, compact, and cost-effective solution for a Class 2 PD or a Class 3 PD.

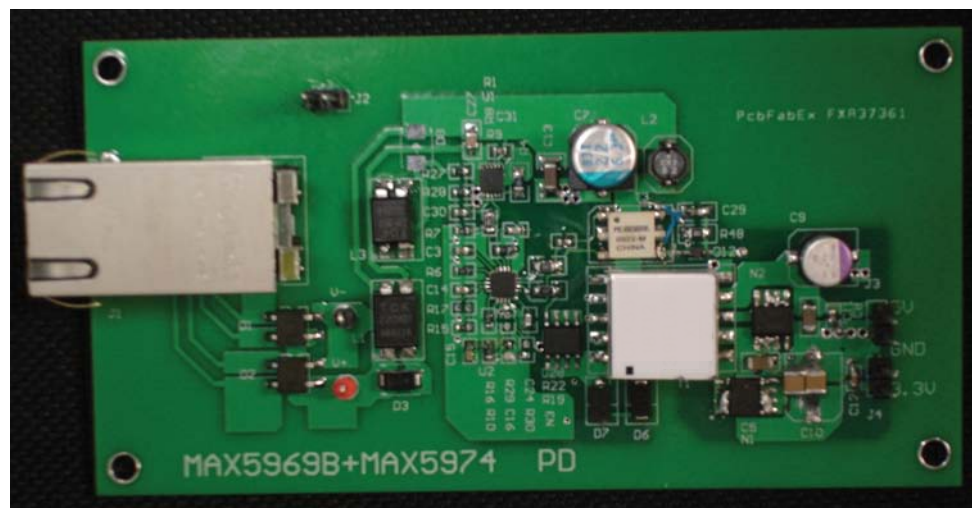
## Specifications:

The 5V/2.6A PD meets the following specifications:









- Input voltage: 36V to 57V
- WAD input voltage: 9V up to 57V
- $V_{OUT}$ : 5V/2.6A
- Output ripples:  $\pm 2\%$
- Load transient  $V_{P-P}$ :  $\pm 2\%$  (50% step-load)
- Line and load regulation:  $\pm 0.2\%$
- Total efficiency with a load of 2.5A at 5V and a 48V input: 87.4% (not including input LAN transformer and diode bridge)



Top view of the reference design.

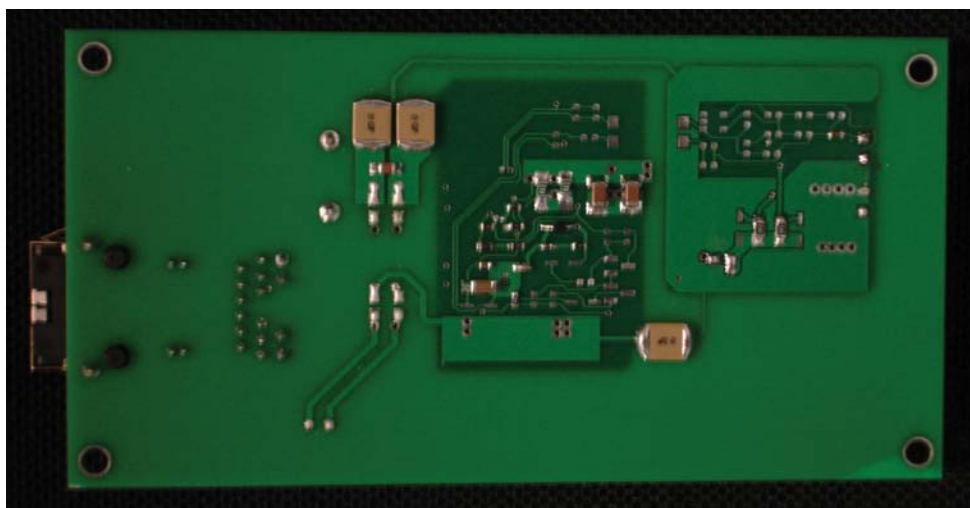

Bottom view of the reference design.

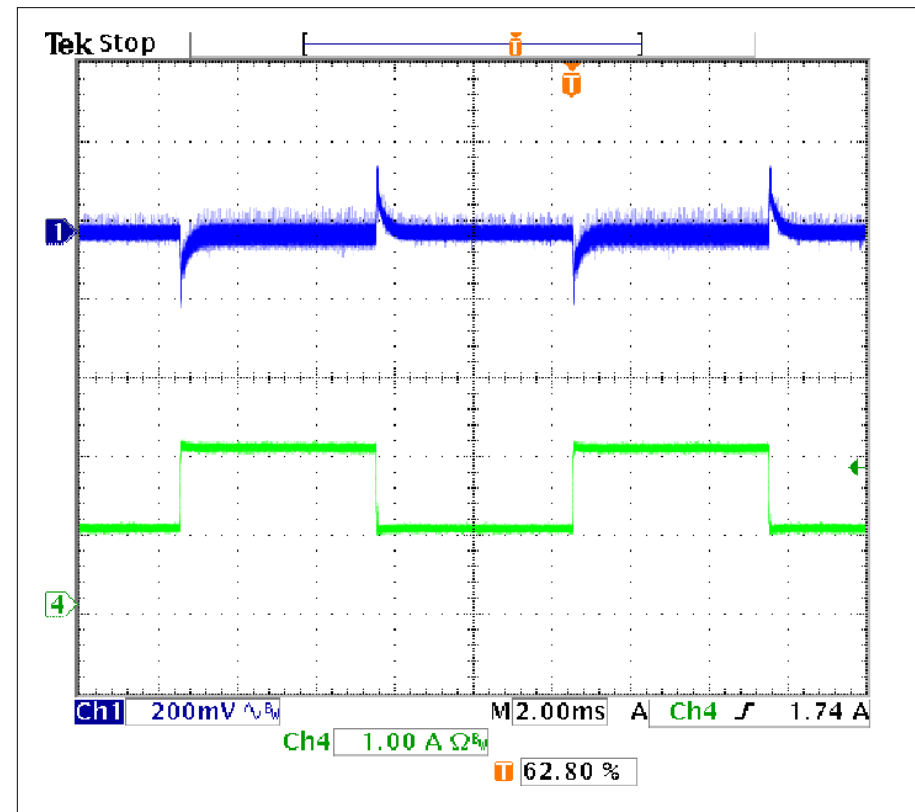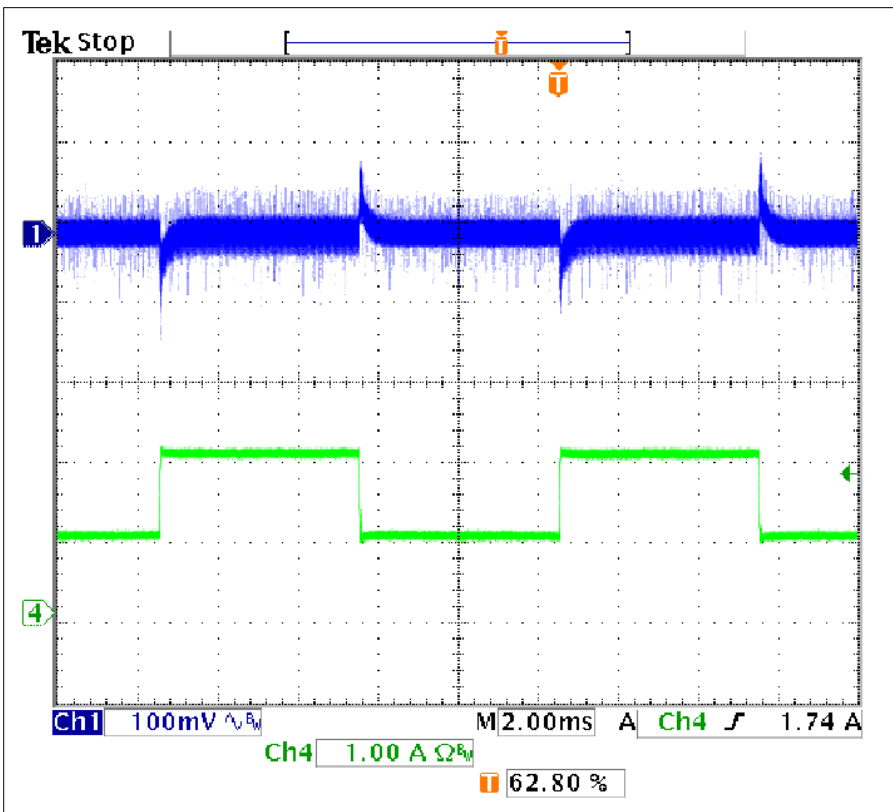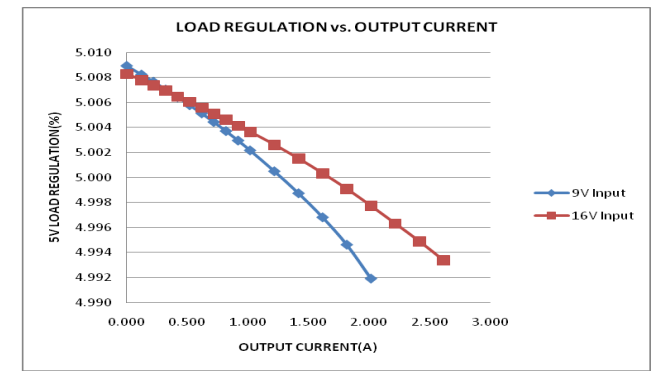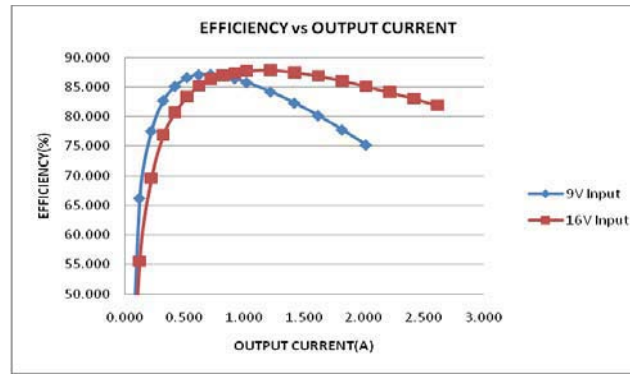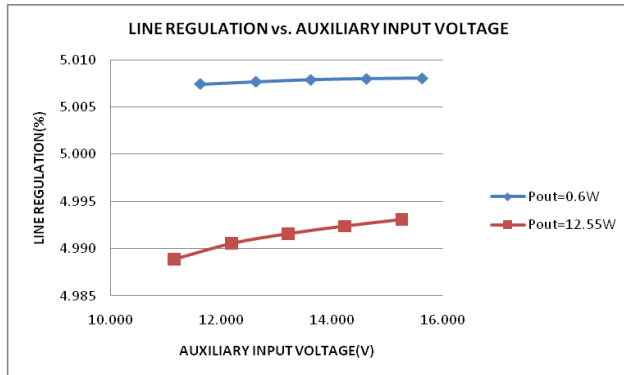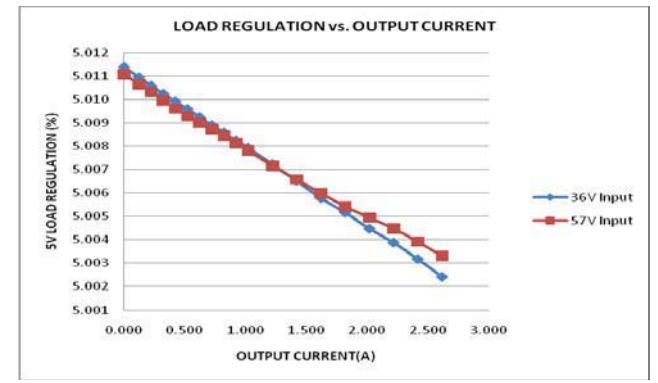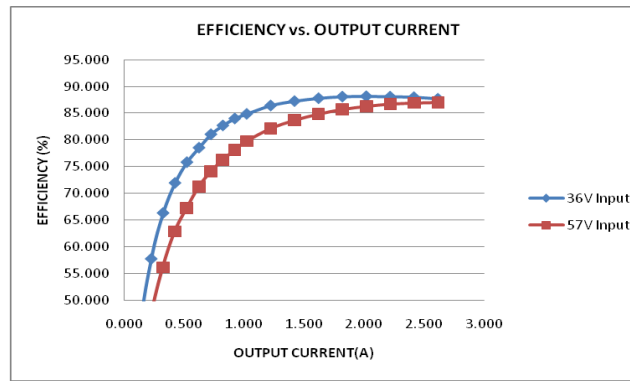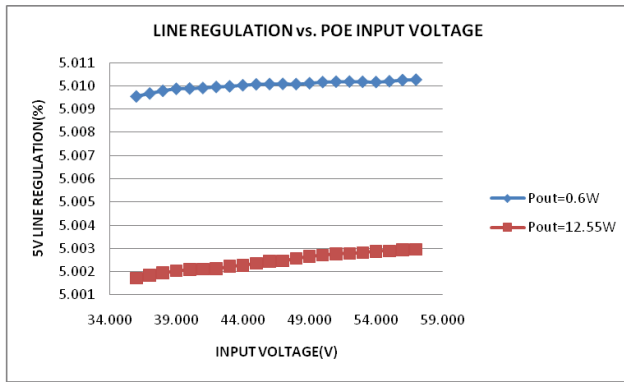


### Transient Response

$V_{IN} = 40V$ ,  $I_{OUT2} = 1A-2.5A$   
 Ch1: 100mV/div, 5V output voltage  
 Ch4: 1A/div, output current  
 Time base: 2ms/div
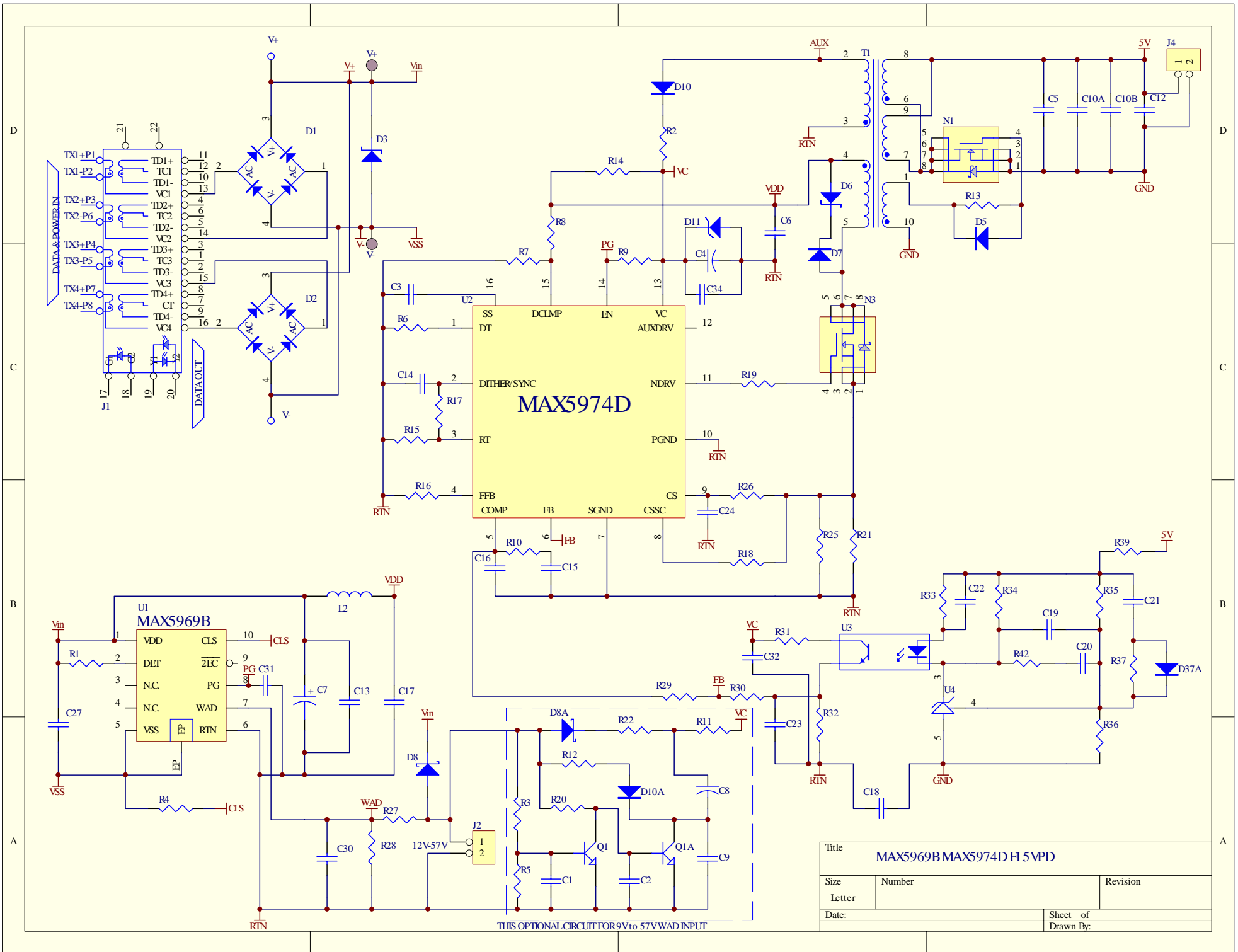
### Transient Response

$V_{IN} = 16V$ ,  $I_{OUT2} = 1A-2.5A$   
 Ch2: 200mV/div, 5V output voltage  
 Ch4: 1A/div, output current  
 Time base: 2ms/div



Title <b>MAX5969B MAX5974D FL5 VPD</b>		
Size	Number	Revision
Letter		
Date:	Sheet of	
	Drawn By:	

IEEE is a registered service mark of the Institute of Electrical and Electronics Engineers, Inc.

---

#### Related Parts

[MAX5969B](#) IEEE 802.3af/at-Compliant, Powered Device Interface Controllers with Integrated Power MOSFET

[MAX5974D](#) Active-Clamped, Spread-Spectrum, Current-Mode PWM Controllers

---

#### Automatic Updates

Would you like to be automatically notified when new application notes are published in your areas of interest? [Sign up for EE-Mail™](#).

---

Application note 4983: [www.maxim-ic.com/an4983](http://www.maxim-ic.com/an4983)

More information

For technical support: [www.maxim-ic.com/support](http://www.maxim-ic.com/support)

For samples: [www.maxim-ic.com/samples](http://www.maxim-ic.com/samples)

Other questions and comments: [www.maxim-ic.com/contact](http://www.maxim-ic.com/contact)

---

AN4983, AN 4983, APP4983, Appnote4983, Appnote 4983

Copyright © by Maxim Integrated Products

Additional legal notices: [www.maxim-ic.com/legal](http://www.maxim-ic.com/legal)